



1. a. **Design** a common bus system between 4 registers (R1, R2, R3 and R4) each of 4-bits using tri-state buffers and decoders.

Answer:

- b. Starting from an initial value of R = 11001001, **determine** the sequence of binary values in R after a logical shift-left, followed by a circular shift-right, followed by a logical shift-right and a circular shift-left.

Answer:


Micro-operation	R
Initially	11001001
R ← shl R	10010010
R ← cir R	01001001
R ← shr R	00100100
R ← cil R	01001000

- c. A digital computer has a common BUS system for 4 registers of 16-bit each; this bus system uses MUXs and a decoder to allow data transfer between any two registers at a time. For this system do the following:
- How many multiplexers are there in the bus?
16 MUXs
 - What is the size of each multiplexer?
4X1 MUX's

2. **Design** an arithmetic circuit with one selection variable S and two n -bit data inputs A and B . The circuit generates the following 4 arithmetic operations in conjunction with the input carry C_{in} . **Draw** the logic diagram for the first two stages.

S	$C_{in}=0$	$C_{in}=1$
0	$D = A+B$ (add)	$D=A+1$ (increment)
1	$D = A-1$ (decrement)	$D=A+B'+1$ (subtract)

Answer:

 

3. The following control inputs are active in the bus system shown in Fig.(1). For each case, **specify** the register transfer that will be executed during the next clock transition

	S2	S1	S0	LD of register	Memory	Adder
a.	1	1	1	IR	Read	--
b.	1	1	0	PC	--	--
c.	1	0	0	DR	Write	--
d.	0	0	0	AC	--	Add

Answer:

Question	S2	S1	S0	LD of register	Memory	Adder	Solution
A	1	1	1	IR	Read	---	$IR \leftarrow M[AR]$
B	1	1	0	PC	---	---	$PC \leftarrow TR$
C	1	0	0	DR	Write	---	$DR \leftarrow AC, M[AR]$ $\leftarrow AC$
d	0	0	0	AC	---	Add	$AC \leftarrow AC + DR$

4. Consider the basic computer registers connected to a common bus system shown in Fig.(1). For each indicated micro-instruction, **complete** the following table:

Microinstruction	Bus select			Source Register	Destination Register			Memory		
	S2	S1	S0		Name	LD	INR	CLR	Read	Write
AR ← PC	0	1	0	PC	AR	1	0	0	0	0
PC ← PC+1	0	1	0	PC	PC	0	1	0	0	0
IR ← M[AR]	1	1	1	M	IR	1	0	0	1	0
AR ← IR	1	0	1	IR	AR	1	0	0	0	0
DR ← M[AR]	0	1	1	M	DR	1	0	0	1	0
TR ← 0	0	0	0	TR	TR	0	0	1	0	0

5. The register transfer statements for a register R and the memory in a computer are as follows (the X's are control functions)

$X_3'X_1$:	R	\leftarrow M[AR]	Read Memory word into R
$X_1'X_2$:	R	\leftarrow AC	Transfer AC to R
$X_1'X_3$:	M[AR]	\leftarrow R	Write R to Memory

The memory has data inputs, data outputs, address inputs, and control inputs to read and write. **Draw the hardware implementation of R and the memory in block diagram form.**

Answer:

