



Benha University	Time: 3 hours	 
Benha Faculty of Engineering	Forth Year : 14/1/2018	
Subject: Electrical drive systems (E1439)	Elect.Eng.Dept.	

Solve & draw as much as you can (questions in two pages)

Question (1)

[15] Points

- a-Define: Electrical drive- Mechanical transformer? [2] points
- b-Explain in details the Speed control of DC motors? [4] points
- c-Write the common types of electrical drives? [2] points
- d-Write the main parts of the electrical drive? [2] points

e-A three phase- Y- induction motor has [380V, 60Hz, 1700rpm, pf=0.85, $\eta_m=0.8$, 4 poles, $J_m = 0.5 Nm \cdot S^2$]. It is used to drive two loads together. The first load is of rotational motion [$J_L = 2 Nm \cdot S^2$, 100Nm, 1000 rpm across a gear box of $\eta_{gear} = 0.9$]. The second load is of linear (motion) lifting 1000Kg to 50m in a one minute across a tool has $\eta_{tool} = 0.7$.

Find ω_s , S, I_s , P_m , T_{equ} , J_{equ} ? [5] points

Question (2)

[15] Points

- a- Draw the block diagram of the closed loop control system used for speed control of a separately excited DC motor and write $\frac{\omega_r}{-T_L}, \frac{\omega_r}{V_r}$? [6] points
- b- A separately excited DC motor [50KW, 240V, 1700rpm, $R_a = 0.1\Omega$, $B = 0.03K\Phi = 1.3 V \cdot S/rad$]. The gain of the speed sensor is 95mV/rad/s. It used the close loop technique to control the motor speed. The field current is held constant.
- i- Find V_r required to drive the motor at rated speed with no load? [3] points
- ii- Find the motor speed when the motor supplied the rated torque and V_r is not changed?
- iii- Find the motor speed if V_r is decreased by 15%? [3] points

Question (3)

[15] Points

A separately excited DC motor has [20hp, 300V, 900rpm, $R_a = 0.25\Omega$, $L_a = 0.05H$, $R_f = 145\Omega$,

$K\Phi = 3.05Nm/A$, $T_{losses} = constant = 1Nm$, load torque = constant = 115Nm].

- a-Find the motor speed if the armature voltage is 200 V? [5] points

b-If its armature is supplied by fully controlled single phase rectifier [firing angle = 30 degrees, 312 V, 60Hz AC supply] and assume constant armature current and field current. Draw the power circuit and the wave forms of voltages and currents and find the motor speed and (pf)? [5] points

c-If its field is supplied by a fully-controlled three phase rectifier [firing angle = 52 degrees, Y-208 V, 60Hz AC supply] and assume constant armature current and field current $K\Phi = 2.3Nm/A$. Draw the power circuit and the wave forms of voltages and currents and find the motor speed and the field voltage? [5] points

Question (4)

[15] Points

A separately excited DC motor has [**230V, 1750rpm, $I_{rate} = 74A, R_a = 0.18\Omega, L_a = 2.93mH$**] is driven with the motor armature supplied from class A chopper [**240V dc source, duty cycle is 0.5 and chopping frequency is 0.5 KHz**]. The field current is held constant at the value giving rated operation on 230V. The armature current is the rated value.

i-Find the minimum and maximum armature currents? [5] points

ii-Find the ripple factors of the armature current and the supply current? [5] points

iii- Draw the power circuit and current and voltage waveforms? [5] points

Question (5)

[30] Points

a-Explain how to control the speed of a 3-phase induction motor? [5] points

b-Draw the equivalent circuit of a 3-phase induction motor and find T_{dev} ? [5] points

c-A three phase wye-connected induction motor [460V, 60Hz, 4 poles, 1750 rpm, $R_s = 1.01\Omega, R_r = 0.69\Omega, X_m = 43.5\Omega, X_1 = 1.3\Omega, X_2 = 1.94\Omega, T_L = 100Nm$. The stator of the motor is connected to a 3-phase full wave AC/AC converter.

i-Find the motor speed when the AC/AC converter output voltage is 460V line to line? [3] points

ii-Find the motor speed when the AC/AC converter output voltage is 230V line to line? [3] points

iii-Draw the power circuit and current and voltage waveforms? [4] points

d-If the stator of the motor is connected to a 3-phase six step inverter.

i-Find the required DC supply to run the motor with speed of 1000 rpm? [3] points

ii-Find the required DC supply to run the motor with speed of 1750 rpm? [3] points

iv- Draw the power circuit and current and voltage waveforms? [4] points

Answer Question (1)

[15] Points

a-Define: Electrical drive- Mechanical transformer?

[2] points

It is a system that converts electrical energy to mechanical energy with electronic control and used for controlling the speed, torque and direction of motion of motors.


The mechanical transformer is a device transforms mechanical energy between two parts with different torque and speed such as gear box and chains.

b-Explain in details the Speed control of DC motors?

[4] points

There are two methods are : 1-armature control as speed less than rated value

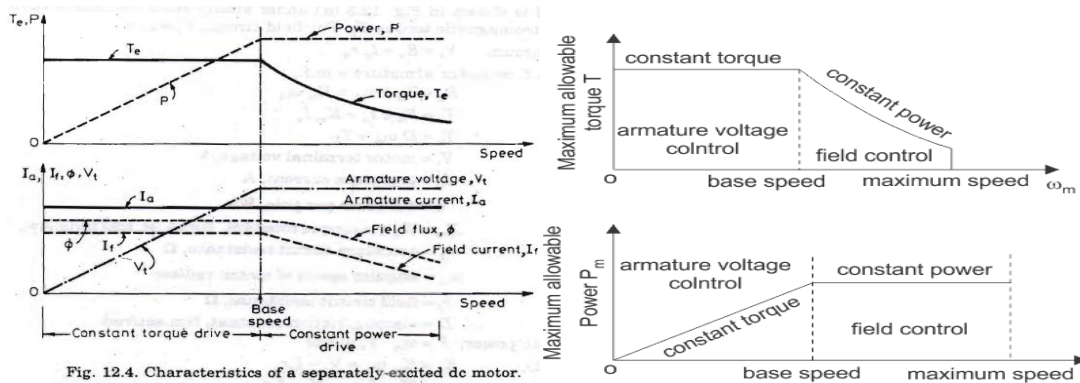
2-field control as speed larger than rated value



the speed of a motor can be controlled by the following methods

1-Armature voltage control 2-Field flux control 3-Armature resistance control

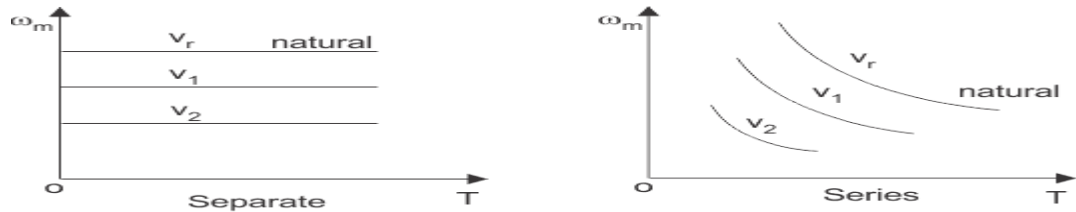
Among all of these, armature voltage control is preferred because of high efficiency and good speed regulation and good transient response. But the only disadvantage of this method is that it can only operate under the rated speed, because the armature voltage cannot be allowed to exceed rated value. The speed torque curve for armature voltage control is shown below.



Armature Voltage Control V_r (rated) > V_1 > V_2

When speed

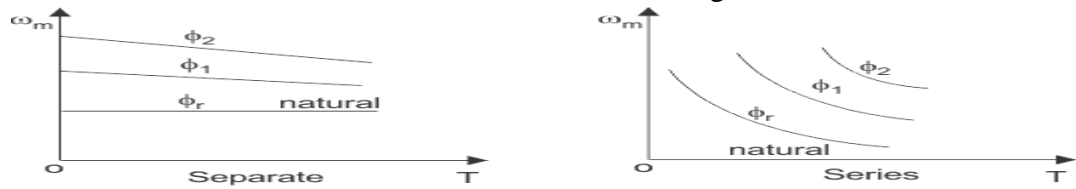
control is required above the rated speed, field flux control is used. Normally in ordinary machines, the maximum speed can be allowed up to twice of the rated speed and for specially designed machines this can be allowed up to six times of the rated speed. The torque speed characteristics for field flux control are shown in the figure below.





Field flux control ϕ_r (rated) > ϕ_1 > ϕ_2


How the

armature voltage control and field flux control is made to operate below and above the rated speed is shown in the figure below. Now, finally coming to resistance control method. Here speed is varied by wasting power in an external [resistor](#) that is connected in series with the armature. This method is not used very much because it is an inefficient method of controlling speed and it is only used in the places where the speed control time forms only a fraction of the total running time, such as traction. The speed torque curve of DC motor drives is given below.

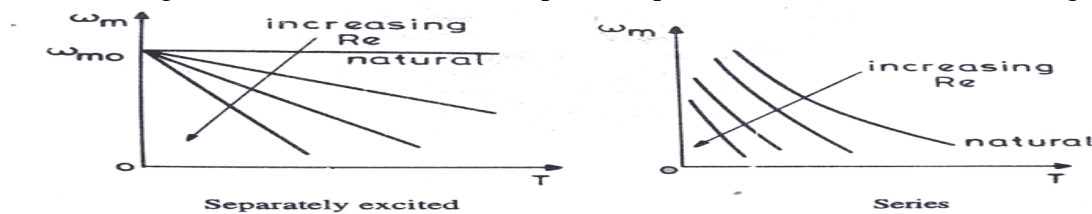
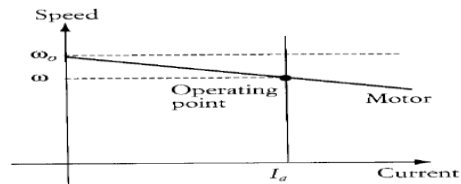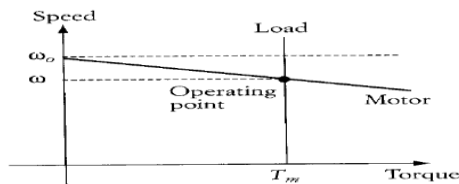
$$\omega = \frac{V_t}{K\phi} - \frac{R_a}{(K\phi)^2} T_d \quad \omega = \frac{V_t}{K\phi} - \frac{R_a I_a}{K\phi}$$



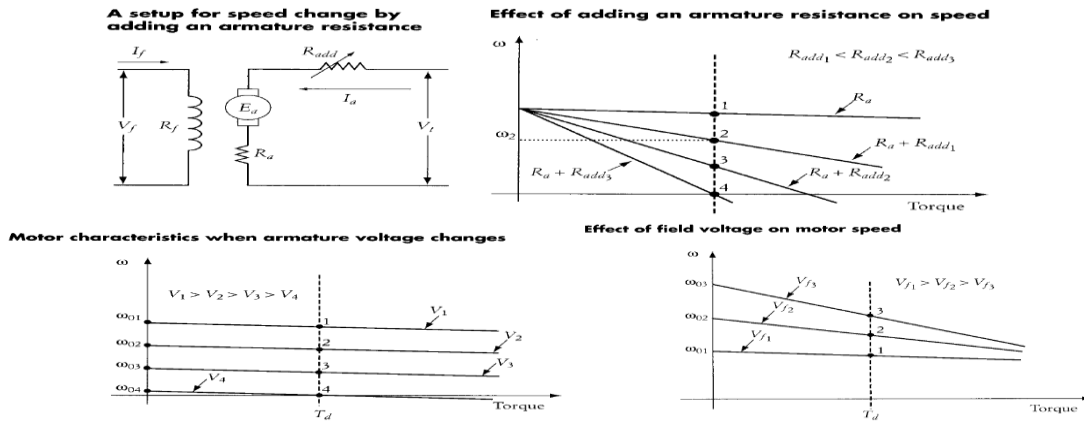

c-Write the common types of electrical drives?

[2] points

2-Types of drive:1- According to motor types:-a) DC drive b) AC drive c) Special drive.

2-According to size:a) large. b) medium. c) small . d)micro drive.

3-According to load connection with motor

a) single motor single load (SMSL) b) multi motor single load(MMSL)

c) single motor multi load(SMML) d) multi motor multi load(MMML)

4-According to control loop types: a-Open loop b- closed loop.

d-Write the main parts of the electrical drive?

[2] points

2.3Main Components of electrical drive system:-

1-main power supply 2-controller with sensor 3-power modulator 4-electrical motor

5-mechanical load with mechanical transformer

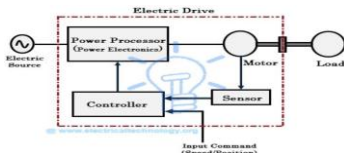


Figure 2.3The block diagram of the electrical drive

e-A three phase- Y- induction motor [380V, 60Hz, 1700rpm, pf=0.85, $\eta_m=0.8$, 4 poles, $J_m = 0.5 Nm \cdot S^2$]. It used to drive two loads together. The first is of rotational motion [$J_L = 2 Nm \cdot S^2$, 100Nm, 1000 rpm across a gear box of $\eta_{gear} = 0.9$]. The second is of linear motion lifting 1000Kg to 50m in one minute across a tool has $\eta_{tool}=0.7$ - Find ω_s , S, I_s , P_m , T_{req} , J_{equ} ?

$$n_s = 120 \cdot 60 / 4 = 1800 \text{ rpm}, \omega_s = 1800 \cdot \pi / 30 = 188.5 \text{ rad/s}, S = (n_s - n_r) / n_s = (1800 - 1700) / 1800 = 0.056$$

$$P_{L1} = T_L \cdot \omega_L = 100 \cdot 1000 \cdot \pi / 30 = 10472 \text{ W}, P_{in \text{ gear}} = P_L / \eta_{gear} = 10472 / 0.9 = 11635.5 \text{ W}$$

$$P_{L2} = F \cdot V = m \cdot g \cdot h / t = 1000 \cdot 9.81 \cdot 50 / 60 = 8175 \text{ W}, P_{in \text{ ele}} = P_L / \eta_{ele} = 8175 / 0.7 = 11678.57 \text{ W}, P_{req} = P_{L1} + P_{L2} = 23314 \text{ W}$$

$$P_{in \text{ m}} = P_{out \text{ m}} / \eta_m = (11635.5 + 11678.57) / 0.8 = 29196.4 \text{ W} = \sqrt{3} V_L I_L \cos \Phi, I_L = 29196.4 / (\sqrt{3} \cdot 380 \cdot 0.85) = 52.2 \text{ A}$$

$$J_{eq} = J_m + J_{I1} \left(\frac{\omega_L}{\omega_m} \right)^2 + M_{I2} \left(\frac{V_L}{\omega_m} \right)^2 = 0.5 + 2 \cdot \left(\frac{1000}{1700} \right)^2 + 1000 \cdot \left(\frac{50}{1700 \cdot (\pi / 30)} \right)^2 = 0.5 + 0.692 + 0.022 = 1.214 \text{ N.m.sec}^2$$

$$T_{req} = P_{req} / \omega_m = 23314.07 / (1700 \cdot (\pi / 30)) = 131 \text{ Nm}$$

Q2a- The closed loop control system is used for speed control of a separately excited DC motor. Draw the steady state block diagram and write $\frac{\omega_r}{V_r} = \frac{K_1 K \phi}{BR_a + K \phi (K_1 K_2 + K \phi)}$ $\frac{\omega_r}{-T_w} = \frac{R_a}{BR_a + K \phi (K_1 K_2 + K \phi)}$

1.1 Mathematical model

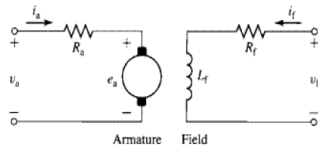


Figure (1) Equivalent Circuit of Separately Excited Dc Motor.

$$v_a = i_a R_a + L_a \frac{d i_a}{dt} + e_b, \quad \text{Armature Equation}$$

$$v_f = i_f R_f + L_f \frac{d i_f}{dt} \quad \text{Field Equation,}$$

$$T = K \phi i_a = T_l + B \omega + J \frac{d \omega}{dt} \quad \text{Mechanical Equation}$$

1.2 Laplace transform with zero initial condition 3- Armature control to separately dc motor.

$$V_a(s) = I_a(s)(R_a + sL_a) + k\phi W(s),$$

$$V_f(s) = I_f(s)(R_f + sL_f)$$

$$T(s) = K\phi I_a(s) = T_l(s) + W(s)(B + Js)$$

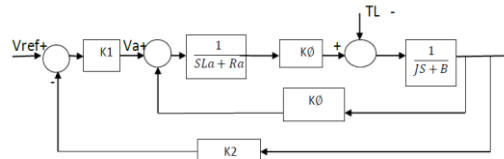


Figure (3) Closed Loop Block Diagram of Separately Excited Dc Motor.

$$\frac{W(s)}{V_{ref}(s)} = \frac{k_1 K \phi}{JL_a s^2 + (JR_a + \beta L_a)S + \beta R_a + K\phi(K\phi + K_1 K_2)}$$

$$\frac{W(s)}{T_l(s)} = \frac{-(R_a + sL_a)}{JL_a s^2 + (JR_a + \beta L_a)S + \beta R_a + K\phi(K\phi + K_1 K_2)}$$

Steady State Analysis. (S=0)

$$\frac{W(s)}{V_{ref}(s)} = \frac{K_1 K \phi}{\beta R_a + K\phi(K\phi + K_1 K_2)}$$

$$\frac{W(s)}{T_l(s)} = \frac{-R_a}{\beta R_a + K\phi(K\phi + K_1 K_2)}$$

b- A [50KW, 240V, 1700 rpm] separately excited DC motor [50KW, 240V, 1700rpm, $R_a = 0.1\Omega$, $B = 0.03 N.m.s/rad$] is controlled by a power converter has a gain =100. The gain of the speed sensor is 95mV/rad/s. It used the close loop technique to control the motor speed. The field current is held constant at a value for which $K\phi = 1.3 V.S/rad$.

i- Find V_r required to drive the motor at rated speed with no load? [3] points

ii- Find the motor speed when the motor supplied the rated torque and V_r is not changed? [3] points

iii- Find the motor speed if V_r is decreased by 15%? [3] points

i- $P=T \omega = (2\pi/60)(1700 * T) = 50000$, $T=281Nm$, rated speed=1700rpm=178rad/s.

$$\frac{\omega_r}{V_r} = \frac{K_1 K \phi}{BR_a + K \phi (K_1 K_2 + K \phi)} = \frac{100 * 1.3}{13.9785} = 9.3, V_r = \frac{178}{9.3} = 19.14V$$

$$\frac{\Delta \omega_r}{-\Delta T_w} = \frac{R_a}{BR_a + K \phi (K_1 K_2 + K \phi)} = \frac{0.1}{14} = 0.007, \Delta \omega_r = -0.007 * 281 = -\frac{2rad}{s}$$

$$\omega_r = 178 - 2 = \frac{176.rad}{s} = 1680.7rpm$$

iii-As V_r decreased to $=0.85 * 19.14 = 16.3V$, $w_r = 16.3 * 9.3 = 151.3rad/s$

As motor loaded then $w_r = 151.3 - 2 = 149.3rad/s = 1425.7rpm$

Q3- A separately excited DC motor has [20hp, 300V, 900rpm, $R_a = 0.25\Omega$, $L_a = 0.05H$, $R_f = 145\Omega$, $K\Phi = 3.05Nm/A$, $T_{losses} = constant = 1Nm$, load torque = constant = 115Nm].

a-Find the motor speed if the armature voltage is 200 V?

[5] points

b-If its armature is supplied by fully controlled single phase rectifier [firing angle = 30 degrees, 312 V, 60Hz AC supply] and assume constant armature current and field current. Draw the power circuit and the wave forms of voltages and currents and find the motor speed and (pf)?

[5] points

c-If its field is supplied by a fully-controlled three phase rectifier [firing angle = 52 degrees, Y-208 V, 60Hz AC supply] and assume constant armature current and field current $K\Phi = 2.3Nm/A$. Draw the power circuit and the wave forms of voltages and currents and find the motor speed and the field voltage? [5] points




a- $I_a = [115 + 1] / 3.05 = 38A$, $E_a = 200 - 38 * 0.25 = 187.4V$, $\omega = 187.4 / 3.05 = 62.46 rad/s$, $n = 596.4 rpm$, $V_a = E_a + I_a R_a$

b-For a single phase rectifier with continuous armature current $V_a > E_a$

$\alpha = 30$ degrees, $V_a = [2V_{max} \cos\alpha] / \pi = (2 * 312 * 1.414 \cos 30) / \pi = 243.3V$, $\omega = [243.3 - 38 * 0.25] / 3.05 = 76.7 rad/s$, $n = 732 rpm$, $V_a = E_a + I_a R_a$, $pf = \cos\alpha = 0.9 \cos 30 = 0.78$, $pf_1(\text{fundamental}) = \cos\alpha = \cos 30 = 0.87$

c-For a three phase rectifier with continuous field current

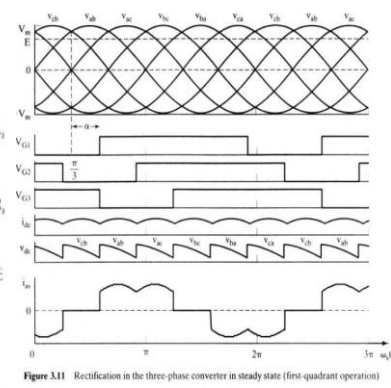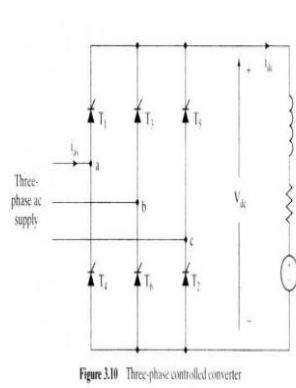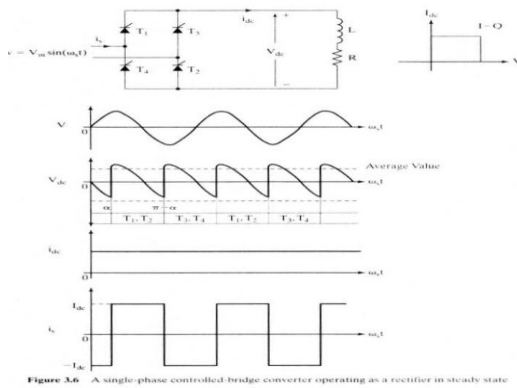$\alpha = 52$ degrees, $V_a = [3V_{max} \cos\alpha] / \pi = (3 * 208 * 1.414 \cos 52) / \pi = 173V$, $\omega = [300 - 38 * 0.25] / 2.3 = 20126.3 rad/s$, $n = 1206 rpm$, $V_a = E_a + I_a R_a$, $pf = \cos\alpha = 0.955 \cos 52 = 0.59$, $pf_1(\text{fundamental}) = \cos\alpha = \cos 52 = 0.62$



Question (4)

[15] Points

A separately excited DC motor has [230V, 1750rpm, $I_{rate} = 74A$, $R_a = 0.18\Omega$, $L_a = 2.93mH$] is driven with the motor armature supplied from class A chopper and 240V dc source. The chopping frequency is 0.5 KHz and the duty cycle=0.5. The field current is held constant at the value giving rated operation on 230V. The armature current is the rated value and assumed to be continuous.

i-Find the minimum and maximum armature currents?

[5] points

ii-Find the ripple factors of the armature current and the supply current?

[5] points

iii- Draw the power circuit and current and voltage waveforms?

[5] points

$$w=1750\text{rpm}=183.3\text{rad/s}, K\Phi = \frac{230-74*0.18}{183.3} = 1.182 \text{ V.S/rad}, E(\text{rate})=1.182*183.3=216.7\text{V}, \text{ as } K=0.5 \text{ and}$$

$$\text{continuous current then } V=0.5*240=120\text{V}, E=120-74*0.18=106.68\text{V}, E/V_{dc}=106.68/240=0.4445,$$


$$T_a=L_a/R_a=0.00293/0.18=0.0163\text{S}, T_p=1/500=2\text{mS}, T_p/T_a=0.123, t_{on \text{ critical}} = \tau \ln \left[1 + \frac{E}{V_{dc}} \left(e^{T_p/\tau} - 1 \right) \right] =$$

$$0.92\text{msec. } K_{\text{critical}} = \frac{\tau}{T_p} \ln \left[1 + \frac{E}{V_{dc}} \left(e^{T_p/\tau} - 1 \right) \right] = 0.461, K=t_{on}/T_p=V_{av}/V_{dc}=120/240=0.5 > K_c \text{ then continuous}$$

$$\text{current mode } I_{\text{max}} = \frac{V_{dc}(1-e^{-t_{on}/\tau})}{R_a(1-e^{-T_p/\tau})} - \frac{E}{R_a} = 100\text{A}, \quad I_{\text{min}} = \frac{V_{dc}(e^{-t_{on}/\tau}-1)}{R_a(e^{-T_p/\tau}-1)} - \frac{E}{R_a} = 54\text{A}$$

$$\text{motor current: } I_{\text{ave}}=74\text{A}, I_{\text{rms}}=1.414*V_{dc}/\pi W_0 L_a = 1.414*240/\pi * 2 * \pi * 500 * 0.00293 = 11.74\text{A}, R_F = 11.74/74 = 0.16$$
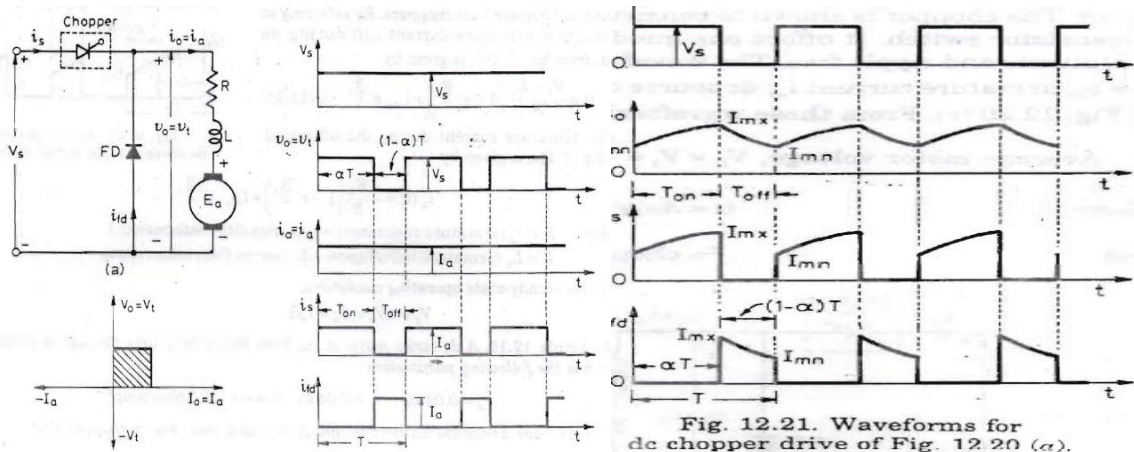
$$\text{Source current: } I_{\text{ave}}=74*K=37\text{A}, I_{\text{rms}}=1.414*I_a/\pi = 1.414*74/\pi = 33.3\text{A}, R_F = 33.3/37 = 0.9$$



Question (5)

[30] Points

a-Explain how to control the speed of a 3-phase induction motor?


[5] points

$n_r=(1-s)n_s, n_s=120f/P$, the speed parameters are frequency, number of poles and slip. The speed is controlled by:


- 1- control the slip
- 2-control the frequency
- 3-control the number of poles.

The slip is controlled by controlling: 4- rotor resistance 5-rotor inductance 6- stator resistance 7-stator inductance 8-magnitude of stator input voltage 9- frequency of stator input voltage 10-inject voltage in the rotor 11-V/f control of the stator voltage. There are three tools: 1-inverter 2-AC/AC converter 3-cycloconverter.

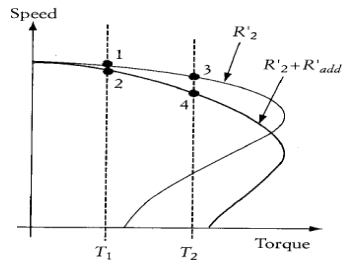
Effect of rotor resistance on motor speed



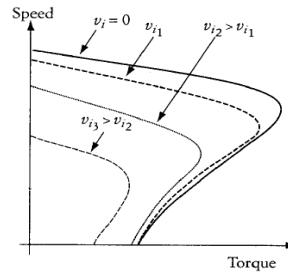
Speed-torque characteristics of induction motor with rotor-injected voltage




Impact of voltage on motor speed

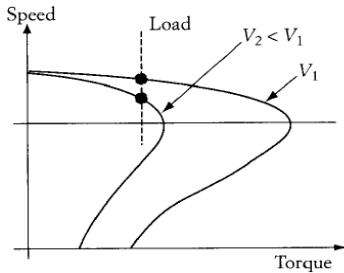

Impact of frequency on motor speed

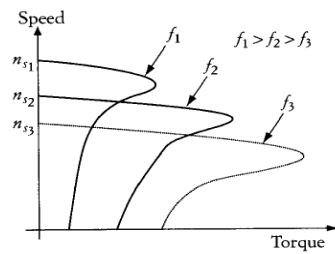

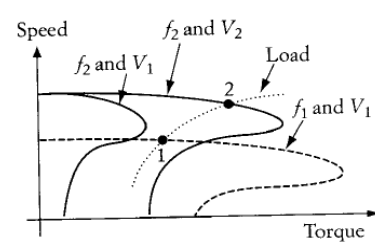Impact of change in frequency and voltage



b-Draw the equivalent circuit of a 3-phase induction motor and find T_{dev} ? [5] points

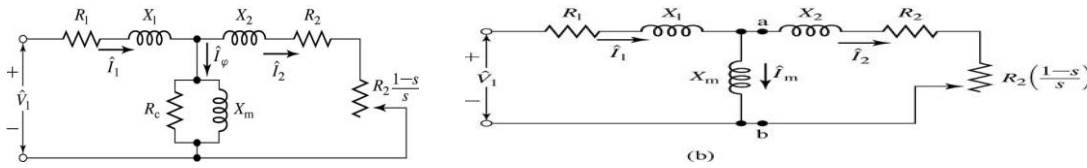


Figure 6.9 Single-phase equivalent circuit for a three-phase induction motor.

$$T_d = \frac{P_d}{\omega} = \frac{V^2 R'_2}{s \omega_s \left[\left(R_1 + \frac{R'_2}{s} \right)^2 + X_{\sigma q}^2 \right]}$$

c-A three phase wye-connected induction motor [460V, 60Hz, 4 poles, 1750 rpm, $R_s = 1.01\Omega$, $R_r = 0.69\Omega$, $X_m = 43.5\Omega$, $X_1 = 1.3\Omega$, $X_2 = 1.94\Omega$, $T_L = 100Nm$. The stator of the motor is connected to a 3-phase full wave AC/AC converter.

i-Find the motor speed when the AC/AC converter output voltage is 460V line to line? [3] points

ii-Find the motor speed when the AC/AC converter output voltage is 230V line to line? [3] points

iii-Draw the power circuit and current and voltage waveforms? [4] points

$$n_s = 120 \cdot 60 / 4 = 1800 \text{ rpm}, \omega_s = 1800 \cdot \pi / 30 = 188.5 \text{ rad/sec.}, \omega_r = 1740 \cdot \pi / 30 = 182.2 \text{ rad/sec.}$$



$$\text{motor torque} = \frac{3V^2 S}{R_2 \omega_s} = \text{load torque} = 100Nm = \frac{460^2 S}{0.96 \cdot 188.5'}$$

$$S = 0.0855, n = (1 - 0.0855) \cdot 1800 = 1646 \text{ rpm}$$



$$\text{motor torque} = 100Nm = \frac{230^2 S}{0.96 \cdot 188.5}, S = 0.342, n = (1 - 0.342) \cdot 1800 = 1184.26 \text{ rpm}$$

$$\frac{T_{cont.}}{T_{rate}} = \left[\frac{1 - S_{cont.}}{1 - S_{rate}} \right]^2 = \frac{S_{rate}}{S_{cont.}} \left(\frac{I_{cont.}}{I_{rate}} \right)^2 \quad I_{cont.} = 10.3 \frac{0.444}{0.028} \cdot \left[\frac{1 - 0.444}{1 - 0.028} \right]^2 = 53.44A$$

Phase control of induction motor

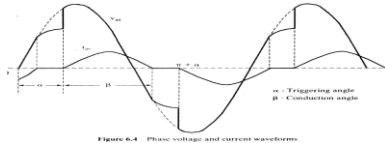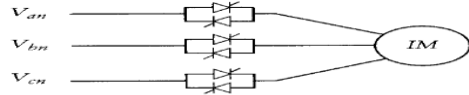

Impact of voltage on motor speed

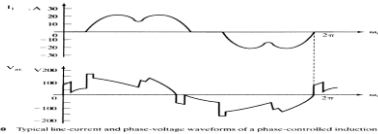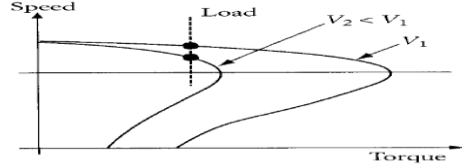

d-If the stator of the motor is connected to a 3-phase six step inverter.

i-Find the required DC supply to run the motor with speed of 1000 rpm and of 1750rpm

iv- Draw the power circuit and current and voltage waveforms?

[4] points

$$S1 = (n_s - n_r) / n_s = (1800 - 1750) / 1800 = 0.028, \omega_{r1} = 1750 * \pi / 30 = 183.3 \text{ rad/sec.}$$

$$S2 = (n_s - n_r) / n_s = (1800 - 1000) / 1800 = 0.444, \omega_{r2} = 1000 * \pi / 30 = 104.72 \text{ rad/sec.}$$

$$\text{motor torque} = \frac{3V^2 s}{R_2 \omega_s} = \text{load torque} = 100 \text{ Nm} = \frac{0.444 * 3V^2}{0.96 * 188.5}, \text{ or } = \frac{0.028 * 3V^2}{0.96 * 188.5}$$

$$\text{for six-step inverter } V_{ph} = \sum_{n=6k \pm 1}^{\infty} \frac{2 * V_{dc}}{n * \pi} \sin n \omega t, V_{1-ph-rms} = \frac{\sqrt{2} * V_{dc}}{\pi}$$

$$V_{1.ph.rms} = 116.6 \text{ V} = 1.414 * \frac{V_{dc}}{\pi}, V_{dc} = 259 \text{ V or } V_{ph-rms} = 116.6 \text{ V} = 1.414 * \frac{V_{dc}}{3}, V_{dc} = 247.35 \text{ V}$$

$$V_{1.ph.rms} = 464.14 \text{ V} = 1.414 * \frac{V_{dc}}{\pi}, V_{dc} = 1031 \text{ V or } V_{ph-rms} = 464.14 \text{ V} = 1.414 * \frac{V_{dc}}{3}, V_{dc} = 984.3 \text{ V}$$

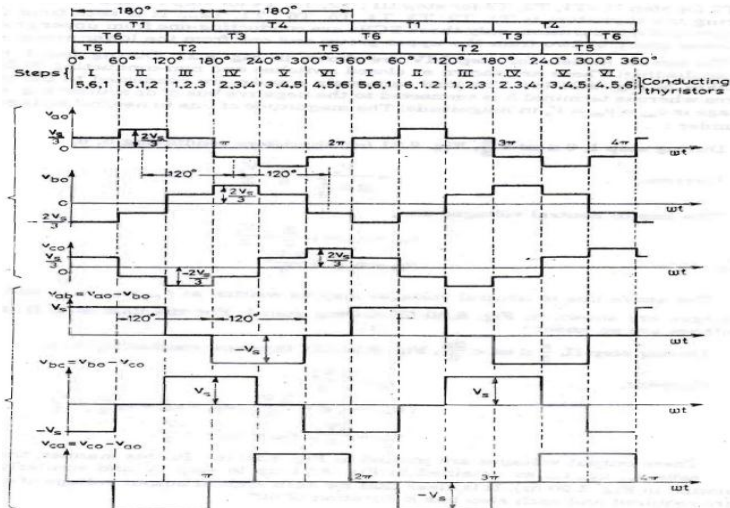
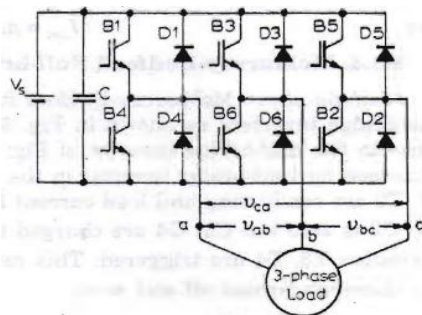


Fig. 8.20. Voltage waveforms for 180° mode 3-phase VSI.